

# Electronic Devices & Circuits II - EE 3EJ4

## Lab #1

-

Stefan Tosti - Tostis - 400367761 - L08  
2023 - 09 - 29

## Questions for Part 1

### Q1. (7 Points)

V+ (VCC)	V- (VE)	V(Q1C) (Volt)	V(Q1B) (Volt)	VCE (Volt)	VBEon (Volt)	RC (ohm)	RB (ohm)	IC (A)	IB (A)	$\beta = IC/IB$	VA  (V)	ro=VA/IC	gm = IC/25mV	r $\pi$ = 25mV/IB
0.5	-1.5	0.397558296	-0.87868933	1.898	0.621	100	1.00E+05	1.02E-03	8.79E-06	117	1000	9.76E+05	4.10E-02	2845

(1)  $V_{BEon} = 0.621V$  and  $I_B = 8.79 \times 10^{-6}A = 8.79\mu A$

(2)  $\beta = 117$

(3)  $|V_a| = 1000V$

(4)  $r_0 = 9.76 \times 10^5 \Omega = 976k\Omega$

(5)  $g_m = 4.10 \times 10^{-2} \frac{A}{mV} = 41mS$

(6)  $r_\pi = 2845 \frac{mV}{A} = 2.845k\Omega$

### Q2. (8 Points)

V+ (VCC)	V- (VE)	Channel 1 (VC)	Channel 2 (VB)	VCE (Volt)	VBEon (Volt)	RC (ohm)	RB (ohm)	IC (A)	IB (A)	$\beta = IC/IB$	VA  (V)	ro=VA/IC	gm = IC/25mV	r $\pi$ = 25mV/IB
0.5	-1.5	0.326	-0.825	1.826	0.675	100	1.00E+05	1.74E-03	8.25E-06	211	213	1.22E+05	6.96E-02	3030

(1)  $I_c = 1.74mA$

(2)  $V_{BEon} = 0.675V$  and  $I_B = 8.25 \times 10^{-6}A = 8.25\mu A$

(3)  $\beta = 211$

(4)  $|V_a| = 213V$

(5)  $r_0 = 1.22 \times 10^5 \Omega = 122k\Omega$

(6)  $g_m = 6.96 \times 10^{-2} \frac{A}{mV} = 69.6mS$

(7)  $r_\pi = 3030 \frac{mV}{A} = 3.03k\Omega$

## Questions for Part 2

### Q3. (7 Points)

V+ (VE)	V- (VCC)	V(Q1C) (Volt)	V(Q1B) (Volt)	VEC (Volt)	VEBon (Volt)	RC (ohm)	RB (ohm)	IC (A)	IB (A)	$\beta = IC/IB$	VA  (V)	ro=VA/IC	gm = IC/25mV	r $\pi$ = 25mV/IB
1.5	-0.5	-0.397093315	0.839935339	1.90	0.660	100	1.00E+05	1.03E-03	8.40E-06	123	143	1.39E+05	4.12E-02	2976

(1)  $V_{BEon} = 0.66V$  and  $I_B = 8.40 \times 10^{-6}A = 8.40\mu A$

(2)  $\beta = 123$

(3)  $|V_a| = 143V$

(4)  $r_o = 1.39 \times 10^5 \Omega = 139k\Omega$

(5)  $g_m = 4.12 \times 10^{-2} \frac{A}{mV} = 41.2mS$

(6)  $r_\pi = 2976 \frac{mV}{A} = 2.976k\Omega$

### Q4. (8 Points)

V+ (VE)	V- (VCC)	Channel 1 (VC)	Channel 2 (VB)	VEC (Volt)	VEBon (Volt)	RC (ohm)	RB (ohm)	IC (A)	IB (A)	$\beta = IC/IB$	VA  (V)	ro=VA/IC	gm = IC/25mV	r $\pi$ = 25mV/IB
1.5	-0.5	-0.3342	0.831	1.83	0.669	100	1.00E+05	1.66E-03	8.31E-06	200	32	1.93E+04	6.63E-02	3008

(1)  $I_c = 1.66mA$

(2)  $V_{BEon} = 0.669V$  and  $I_B = 8.31 \times 10^{-6}A = 8.31\mu A$

(3)  $\beta = 200$

(4)  $|V_a| = 210V$

(5)  $r_o = 1.93 \times 10^4 \Omega = 19.3k\Omega$

(6)  $g_m = 6.63 \times 10^{-2} \frac{A}{mV} = 66.3mS$

(7)  $r_\pi = 3008 \frac{mV}{A} = 3.008k\Omega$

### Questions for Part 3

Q5. (10 Points)

Applying KVL from Base to Emitter yields:

$$V_{BB} - R_{BB} I_B - V_{BE_{on}} - I_E R_3 - V_{EE} = 0 \rightarrow$$

$$V_{BB} - V_{BE_{on}} - V_{EE} = I_B (R_{BB} + (\beta + 1) R_3)$$

$$I_B = \frac{V_{BB} - V_{BE_{on}} - V_{EE}}{R_{BB} + (\beta + 1) R_3}$$

Aside

$$I_C = \beta I_B = \alpha I_E$$

$$\beta I_B = \alpha I_E$$

$$\beta I_B = \frac{\beta}{\beta + 1} I_E$$

$$I_E = (\beta + 1) I_B$$

**Q6. (10 Points)**

Using equation (3): let  $\Delta V_{EE} = V_{EE} + \Delta V_{EE}$

$$I_B + \Delta I_B = \frac{V_{BB} - (V_{EE} + \Delta V_{EE}) + V_{BEon}}{R_{BB}}$$

$$\Delta I_{B1} = \frac{V_{BB} - (V_{EE} + \Delta V_{EE}) + V_{BEon}}{R_{BB}} \quad - (1)$$

Using equation Q5: let  $\Delta V_{EE} = V_{EE} + \Delta V_{EE}$

$$I_B + \Delta I_{B2} = \frac{V_{BB} - (V_{EE} + \Delta V_{EE}) + V_{BEon}}{R_{BB} + (\beta + 1)R_3}$$


$$\Delta I_{B2} = \frac{V_{BB} - (V_{EE} + \Delta V_{EE}) + V_{BEon}}{R_{BB} + (\beta + 1)R_3} \quad - (2)$$

The main difference between these 2 equations is that in equation (3) we do not see the presence of  $R_3$ .

This is because it was taken to be 0, based on  $V_{BEon}$  as obtained in the previous section. In **Q5** we do not consider  $R_3 = 0$  and thus we get the term,  $(\beta + 1)R_3$

Since  $\beta$  is always a positive value, and the resistance,  $R_3$  is also always positive, then we can conclude that the term  $(\beta + 1)R_3$  will be an overall positive value. This means that equations (1) and (2) have the same numerator, but (2) will always have a larger denominator than (1). This means that for all parameters,  $\Delta I_{B2} < \Delta I_{B1}$ . This confirms the idea that the emitter resistor,  $R_3$ , reduces the change in  $I_B$

**Q7. (15 Points)**

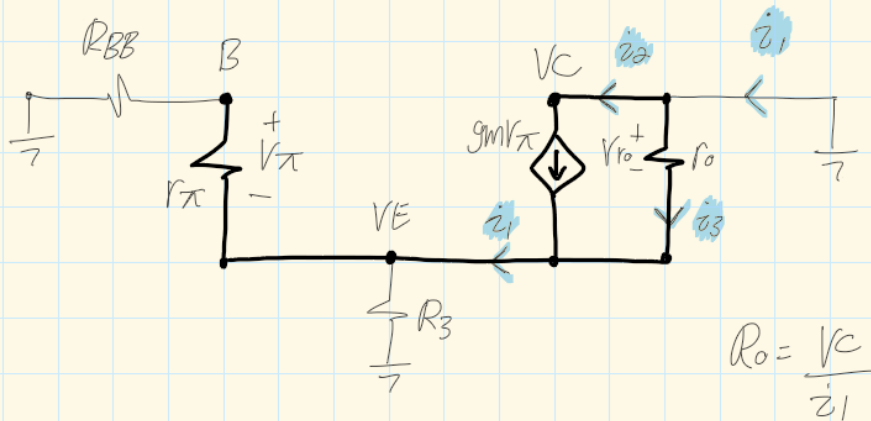

$$i_2 = g_m v_\pi$$

$$i_1 = i_2 + i_3 \Rightarrow i_3 = i_1 - i_2 = i_1 - g_m v_\pi$$

$$v_{ro} = r_o \cdot i_3 = (r_o)(i_1 - g_m v_\pi)$$

$$v_E = (i_1) [(R_{BB} + r_\pi) \parallel R_3]$$

$$v_\pi = -v_E \cdot \frac{r_\pi}{R_{BB} + r_\pi}$$

$$v_C = v_E + v_{ro}$$

$$v_C = (i_1) [(R_{BB} + r_\pi) \parallel R_3] + r_o (i_1 - g_m v_\pi)$$

$$v_C = (\alpha)(i_1) + r_o (i_1 - g_m v_\pi)$$

$$v_C = \alpha i_1 + r_o i_1 + \frac{g_m v_E r_\pi}{R_{BB} + r_\pi} \cdot r_o$$

$$v_C = \alpha i_1 + r_o i_1 + \frac{g_m r_\pi}{R_{BB} + r_\pi} \cdot \alpha i_1 \cdot r_o$$

$\Rightarrow$   $|e| \propto \frac{r_o}{(R_{BB} + r_\pi) \parallel R_3}$

$$\frac{v_C}{i_1} = \alpha + r_o + \frac{g_m r_\pi \cdot \alpha \cdot r_o}{R_{BB} + r_\pi} = R_o$$

$$R_o = r_o + [R_3 \parallel (R_{BB} + r_\pi)] + \frac{g_m r_\pi}{R_{BB} + r_\pi} \cdot [R_3 \parallel (R_{BB} + r_\pi)] \cdot r_o$$

$$R_o = r_o + [R_3 \parallel (R_{BB} + r_\pi)] \left[ 1 + g_m r_o \left( \frac{r_\pi}{R_{BB} + r_\pi} \right) \right]$$

**Q8. (10 Points)**

Since  $R_3 \neq 0$ , we now have to take into account a voltage drop across this resistor. Previously, we had the expression  $V_{o,min} = V_E + 0.3V$ , the resistor,  $R_3$ , has a voltage drop defined by  $V_{R3} = I_e R_3$  and thus we can define a new expression for  $V_{o,min}$ , where  $V_{o,min} = V_E + 0.3V + I_e R_3$

**Q9. (15 Points)**

$$\begin{array}{llll} V_{EE} = -5V & R_3 = ? & \text{from Q1, } \beta = 117 & i_c = \beta i_b = i_e \\ I_o = 1mA = I_c & R_2 = 100k & V_{CE} = 0.3V & \beta i_b = i_e \\ V_{o,min} = -2V & R_1 = ? & & \end{array}$$

$$V_{o,min} = V_{EE} + I_e R_3 + 0.3V \rightarrow I_e = \frac{\beta+1}{\beta} I_c$$

$$R_3 = \frac{V_{R3}}{I_e} = \frac{V_{o,min} - V_{EE} - V_{CE}}{I_e} = \frac{V_{o,min} - V_{EE} - V_{CE}}{\frac{\beta+1}{\beta} \cdot I_c} = \frac{(-2) - (-5) - 0.3}{\left(\frac{118}{117}\right)(1mA)} = 2.67 k\Omega$$

from the given circuits:  $V_{BB} = \frac{R_1}{R_1 + R_2} V_{EE}$ ,  $R_{BB} = R_1 \parallel R_2$

$$I_B R_{BB} + V_B = \frac{R_1}{R_1 + R_2} V_{EE}$$

$$I_B \cdot \frac{R_1 R_2}{R_1 + R_2} + V_B = \frac{R_1}{R_1 + R_2} V_{EE}$$

$$\frac{I_c}{\beta} \cdot \frac{100R_1}{100+R_1} + V_B = \frac{R_1}{100+R_1} (-5) \rightarrow$$


$$\frac{1}{117} \cdot \frac{100R_1}{100+R_1} - 1.686 = \frac{R_1}{100+R_1} (-5)$$

Aside


$$\begin{aligned} V_B &= V_{EE} + I_e R_3 + V_{BE(on)} \\ V_B &= -5 + \left(\frac{118}{117}\right)(2.67) + 0.621 \\ V_B &= -1.686V \end{aligned}$$

$$R_1 = 40.4 k\Omega$$

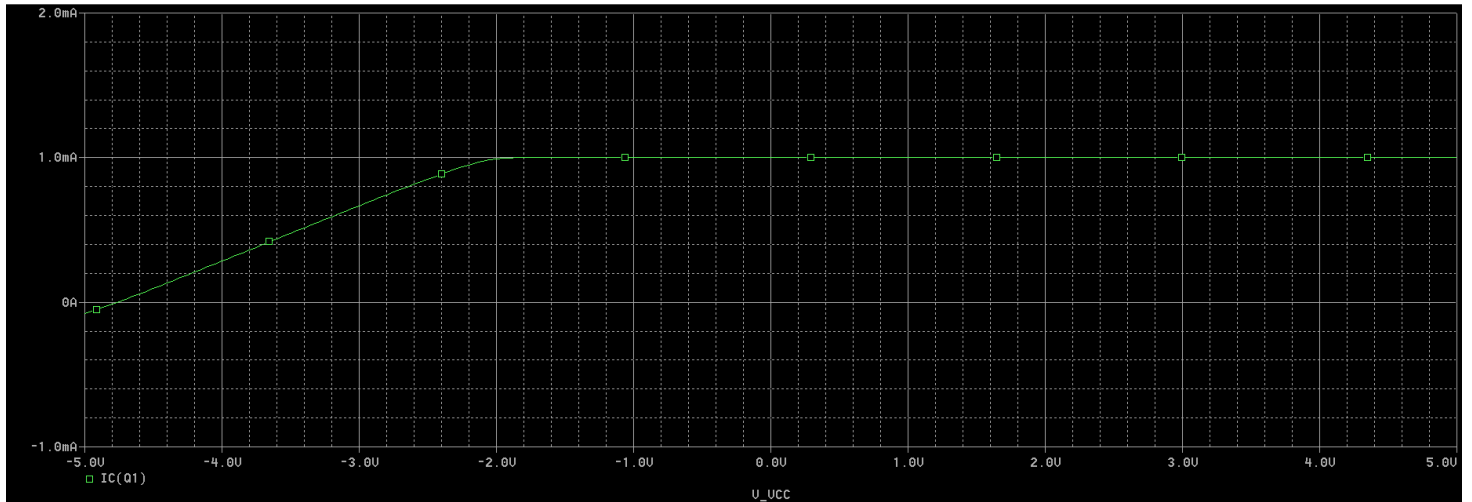The plot of  $I_o$  vs  $V_{cc}$  can be found below



**Q10. (10 Points)**

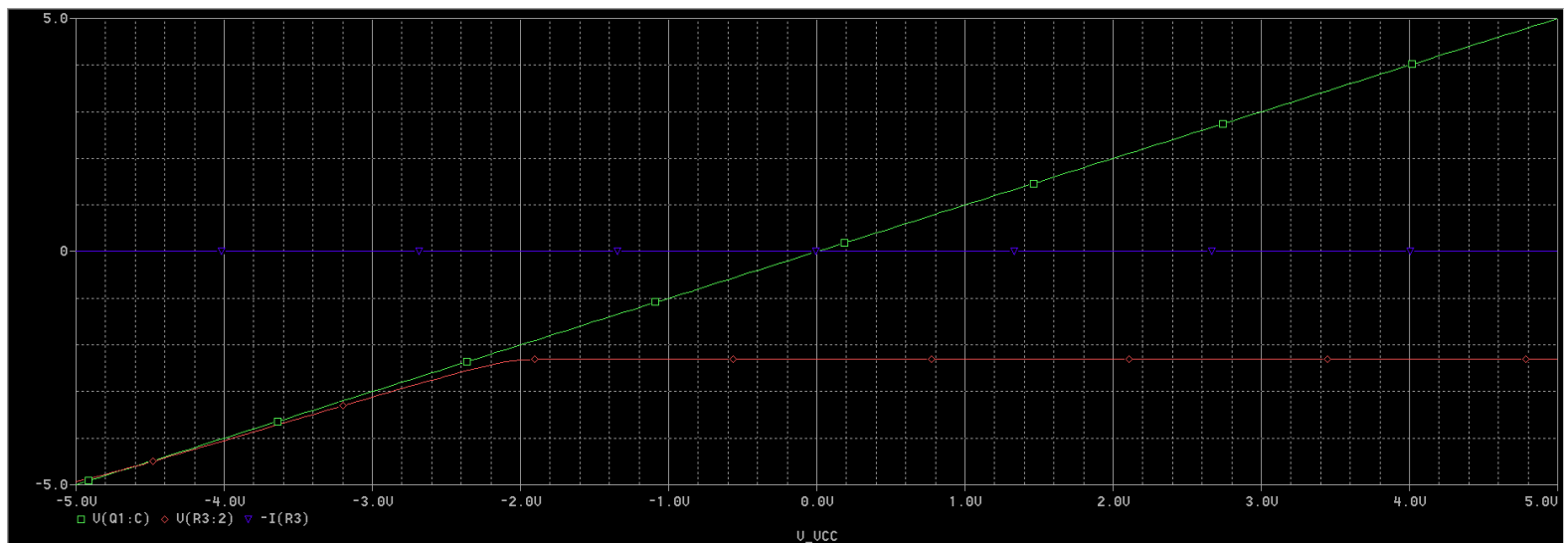

Above is the plot of  $I_c$  (Blue),  $V_{cc}$  (Green) &  $V_E$  (Red)

By generating a plot of  $V_{cc}$  vs  $V_E$  we can determine the  $|V_{CE}|$ . As can be seen from the graph above,  
 $|V_{CE}| = V_{cc} - V_E = (-2V) - (-2.3V) = 0.3V$  and thus we can verify the operating condition that  
 $|V_{CE}| \geq 0.3V$



The circuit used to simulate the above can be found below –

