

Electronic Devices & Circuits II - EE 3EJ4

Lab #5

-

Stefan Tosti - Tostis - 400367761 - L08
2023 - 12 - 04

Questions for Part I

Question 1 - Part 1

We can derive the transfer function as follows...

$$T(s) = \frac{V_o(s)}{V_{in}(s)}, \text{ Recall the ideal op-amp properties; } V_+ = V_- \text{ \& } i_+ = i_- = 0$$

$$V_- = V_o(s) \frac{R_3}{R_2 + R_3}$$

$$\frac{V_{in} - V_+}{R_1} = (sC_1)V_+$$

$$\frac{V_{in} - V_o(s) \frac{R_3}{R_2 + R_3}}{R_1} = (sC_1) \left(V_o(s) \frac{R_3}{R_2 + R_3} \right)$$

$$T(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{R_3 + R_2}{R_3(R_1 s C_1 + 1)}$$

To find the low frequency gain, we can evaluate $T(s)$ @ $s = 0 \dots T(0) = 1.5 = 3.52dB$

We can compute the $-3dB$ frequency as follows... $f_c = \frac{1}{2\pi R_1 C_1} = 1591Hz$

Question 1 - Part 2

For the simulated data in step 1.3...

$$A_V = T(0) = \frac{V_o}{V_{in}} = \frac{150mV}{100mV} = 1.5 \frac{V}{V} = 3.52dB$$

| Frequency | M(V(Vout)) | P(V(Vout)) |
|-----------|-------------|--------------|
| 1 | 0.150000077 | -0.036069295 |

To determine the value of V_o that corresponds to $f_c \dots$

$$20 \log\left(\frac{V_o}{0.1}\right) = 3.52 - 3 \Rightarrow V_o = 0.106V$$

| Frequency | M(V(Vout)) | P(V(Vout)) |
|-------------|-------------|--------------|
| 1577.683204 | 0.106318853 | -44.74587498 |

We can correspondingly find the value of $f_c \dots$

$$f_c = 1577.6832 Hz$$

For the measured data in step 1.8...

$$A_V = T(0) = \frac{V_o}{V_{in}} = \frac{149.7mV}{100mV} = 1.497 \frac{V}{V} = 3.50dB$$

| Frequency | M(V(Vout)) | P(V(Vout)) |
|-----------|------------|------------|
| 1 | 0.1497483 | -0.04507 |

To determine the value of V_o that corresponds to $f_c \dots$

$$20 \log\left(\frac{V_o}{0.1}\right) = 3.50 - 3 \Rightarrow V_o = 0.1059V$$

| Frequency | M(V(Vout)) | P(V(Vout)) |
|-----------|------------|------------|
| 1513.561 | 0.1063753 | -44.1436 |

We can correspondingly find the value of $f_c \dots$

$$f_c = 1513.561 Hz$$

In the above cases, the measured and simulated data match (relatively closely) the data that was obtained from the derived transfer function.

Questions for Part II

Question 2

We can derive the transfer function as follows...

$$T(s) = \frac{V_o(s)}{V_{in}(s)}, \text{ Recall the ideal op-amp properties; } V_+ = V_- \text{ \& } i_+ = i_- = 0$$

Applying KCL at the node between R_1 & R_2 (V_x) ...

$$\frac{V_x - V_{in}}{R_1} + \frac{V_x}{R_2 + sC_2} + \frac{V_x - V_{out}}{sC_1} = 0$$

$$V_- = V_+ = V_{out} \frac{R_3}{R_3 + R_4}$$

Rearranging the above, we obtain...

$$T(s) = \frac{V_o}{V_{in}} = \frac{R_3 + R_4}{s^2(C_1C_2R_1R_2R_3) + s(C_2R_2R_3 + C_2R_1R_3 - C_1R_1R_4) + R_3} = \frac{91 \times 10^6}{s^2 + (15.5 \times 10^3)s + 45.5 \times 10^6}$$

We can then find the desired quantities by comparing the above to the standard form equation...

$$T(s) = \frac{a_o}{s^2 + \frac{\omega_o}{Q}s + (\omega_o)^2}$$

$$\text{Low Frequency gain} = \frac{a_o}{\omega_o^2} = \frac{91 \times 10^6}{45.5 \times 10^6} = 2 \frac{V}{V} = 6.02 \text{ dB}$$

Comparing the above to the simulated data in step 2.2...

| Frequency | DB(V(Vout)) | P(V(Vout)) |
|-----------|-------------|--------------|
| Hz | dBV | Degrees |
| 1 | 6.020586918 | -0.122644171 |

Comparing the above to the measured data in step 2.6...

| Frequency | Manitude | Phase |
|-----------|-------------|--------------|
| Hz | dB | Degrees |
| 1 | 6.009293758 | -0.112854462 |

As we can see, the measured and simulated data agree with the calculated value from our transfer function


Question 3 - Part 1

We can determine the pole frequency by first determining ω_o and then using $\omega_o = 2\pi f_o$


$$f_o = \frac{\omega_o}{2\pi} = \frac{\sqrt{45.5 \times 10^6}}{2\pi} = 1.07 \text{ KHz}$$

The below graphs are plots from the simulated data 2.2 and 2.6 respectively. We can verify our calculated pole frequency above visually by seeing that the pass-band of the filter ends roughly around 1 KHz in both cases

From step 2.2 ...

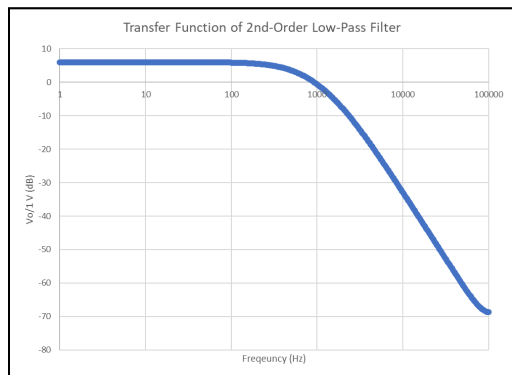

From step 2.6 ...

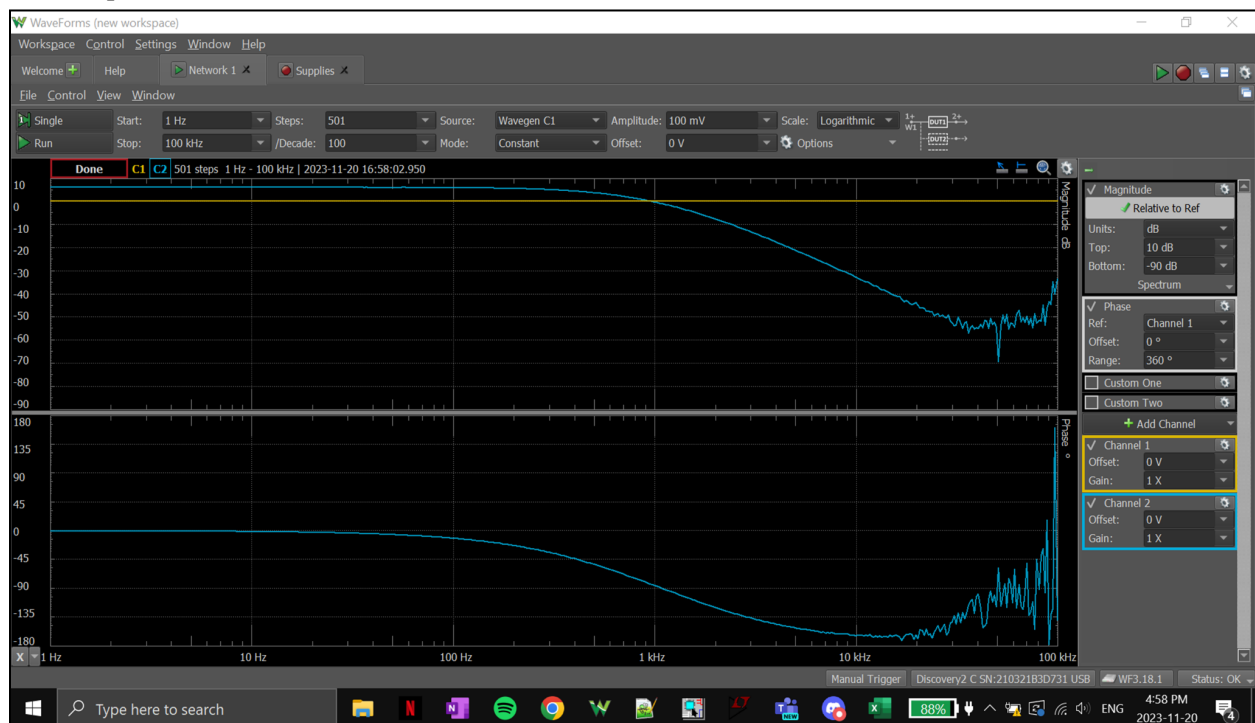

Question 3 - Part 2

We can determine the cut-off frequency, ω_c , as follows...

$$|T(j\omega_c)| = \frac{91 \times 10^6}{\sqrt{(45.5 \times 10^6 - \omega_c^2)^2 + (15.5 \times 10^3)^2 \omega_c^2}} = \sqrt{2}$$

$$\omega_c = 3574.52 \Rightarrow f_c = \frac{3574.52}{2\pi} = 568.9 \text{ Hz}$$

We can verify this data from step 2.2 and 2.6 by examining the frequency at which the gain reaches 3.02dB

For step 2.2 ...

| Frequency | DB(V(Vout)) | P(V(Vout)) |
|-------------|-------------|--------------|
| 565.5555225 | 3.036726579 | -59.17249618 |

For step 2.6 ...

| Frequency | Manitude | Phase |
|-------------|-------------|--------------|
| 588.8436554 | 3.027947597 | -59.54468491 |

Question 3 - Part 3

We can determine the Pole Quality Factor by isolating for Q in our developed transfer function...

$$\frac{\omega_o}{Q} = 15.5 \times 10^3$$

$$Q = \frac{\omega_o}{15.5 \times 10^3} = \frac{\sqrt{45.5 \times 10^6}}{15.5 \times 10^3} = 0.435$$


Question 3 - Part 4

The peak value of the magnitude of the transfer function would be 6.02dB. This occurs because the above Q value is less than 0.707, meaning the system is overdamped and has no “bump” at the pole frequency.

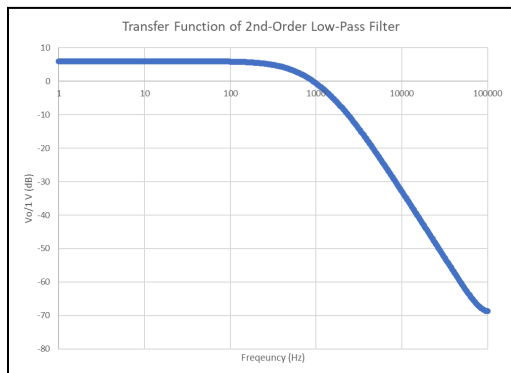
Question 3 - Part 5

The peak value of the transfer function occurs from 0 Hz, and then dropping off at our pole frequency of 1.07 KHz

We can evaluate the results from **Part 4** and **Part 5** by again taking a look at the plotted functions from step 2.2 and 2.6 ...



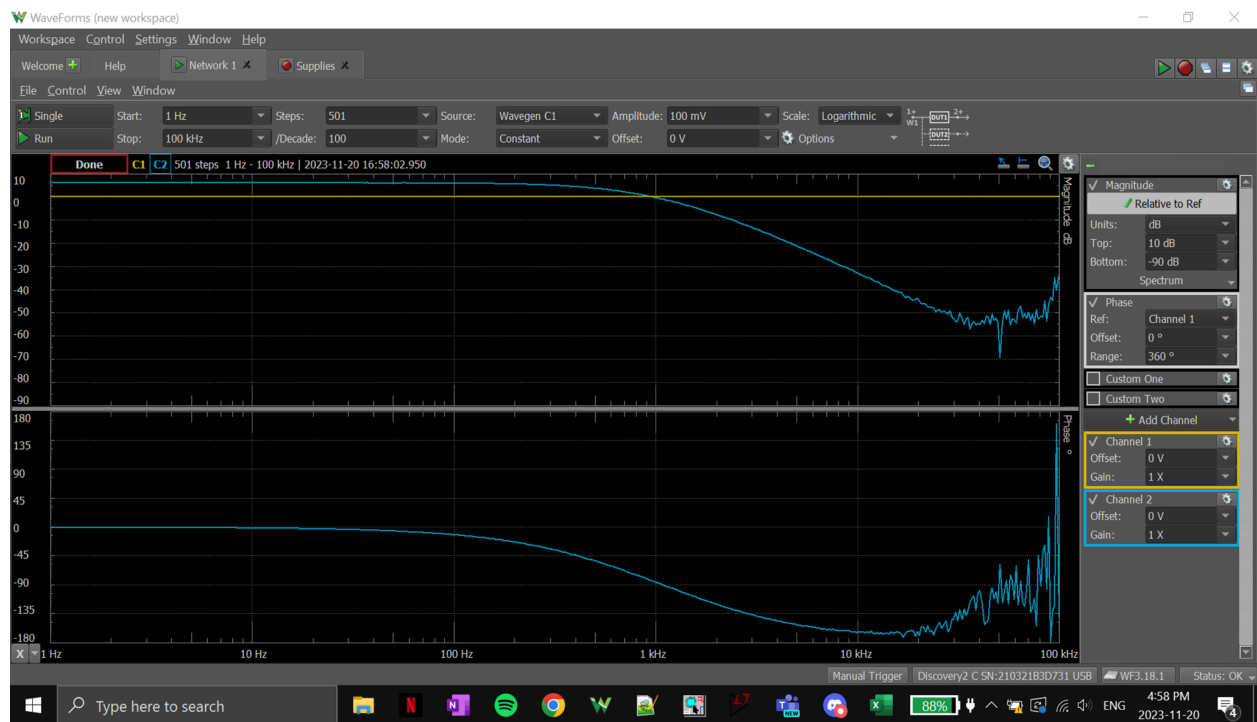From these, we can tell that the magnitude of the gain is maximized at 6.02 dB, starting from 0 Hz, and then dropping off at our pole frequency of 1.07 KHz



Question for Part III

Question 4

We can derive the transfer function as follows...

$$T(s) = \frac{V_o(s)}{V_{in}(s)}, \text{ Recall the ideal op-amp properties; } V_+ = V_- \text{ \& } i_+ = i_- = 0$$

Applying KCL at the common node between C_1 , C_2 , R_2 ...

$$\frac{V_1 - V_{in}}{R_1} + V_1 s C_2 + \frac{V_1 - V_o}{\frac{1}{s C_1}} = 0$$

Rearranging the above, we obtain...

$$T(s) = \frac{V_o}{V_{in}} = \frac{\frac{-s}{R_1 C_1}}{s^2 + s\left(\frac{1}{C_1 R_2} + \frac{1}{C_2 R_2}\right) + \frac{1}{C_1 C_2 R_1 R_2}}$$

In the above, the center frequency is the same as ω_o ...

$$\omega_o^2 = \frac{1}{C_1 C_2 R_1 R_2} \Rightarrow \omega_o = \sqrt{\frac{1}{C_1 C_2 R_1 R_2}} \approx 4166.7 \frac{rad}{s}$$

$$f_o = \frac{\omega_o}{2\pi} = 663 \text{ Hz}$$

Plugging the above value of ω_o into the derived transfer function, we obtain...

$$\text{Center Frequency Gain} = T\left(4166.7 \frac{rad}{s}\right) = -6.02 \text{ dB}, -0.5 \text{ dB}$$

We can verify the above using the data in step 3.2 and 3.6...

| Frequency | DB(V(Vout)) | P(V(Vout)) |
|-------------|--------------|--------------|
| 663.4102514 | -6.020589659 | -180.0370809 |

| Frequency | Manitude | Phase |
|------------|------------|------------|
| 660.693448 | -6.0078727 | 178.733222 |

Question 5 - Part 1

Using the transfer function derived in the previous question, we can obtain the center frequency...

$$\omega_o^2 = \frac{1}{C_1 C_2 R_1 R_2} \Rightarrow \omega_o = \sqrt{\frac{1}{C_1 C_2 R_1 R_2}} \approx 4166.7 \frac{rad}{s}$$

$$f_o = \frac{\omega_o}{2\pi} = 663 \text{ Hz}$$

Question 5 - Part 2

Using the transfer function derived in the previous question, we can determine the pole quality factor ...

$$\frac{\omega_o}{Q} = \frac{1}{C_1 R_2} + \frac{1}{C_2 R_2} \Rightarrow Q = 0.5$$

Question 5 - Part 3

We can determine the 2 pole frequencies as follows...

$$\frac{\frac{-s}{R_1 C_1}}{s^2 + s\left(\frac{1}{C_1 R_2} + \frac{1}{C_2 R_2}\right) + \frac{1}{C_1 C_2 R_1 R_2}} = -9.03dB$$
$$\omega_1 = 1725.9 \frac{rad}{s}, \omega_2 = 10,059.2 \frac{rad}{s}$$

Question 5 - Part 4

We can determine the 3dB bandwidth as follows...

$$BW = \omega_2 - \omega_1 = 8333.3 \frac{rad}{s}$$

We can verify the above measurements as follows, using the data from step 3.2 and 3.6...

| Frequency | DB(V(Vout)) | P(V(Vout)) |
|-------------|--------------|-------------|
| 272.6738966 | -9.075976901 | -134.708069 |

| Frequency | DB(V(Vout)) | P(V(Vout)) |
|-------------|--------------|-------------|
| 1614.064152 | -9.081884151 | -225.357865 |

| Frequency | Manitude | Phase |
|-----------|------------|------------|
| 269.15348 | -8.9916308 | -136.16922 |

| Frequency | Manitude | Phase |
|-----------|------------|------------|
| 1621.8101 | -9.1015004 | 132.758679 |